Pocket Guide to Watthour Meters



Steve Hudson, P.E. VP of Hardware Engineering

10737 Lexington Drive Knoxville, TN 37932 Phone: (865) 966-5856

www.powermetrix.com



Overview of the Pocket Guide

- Chapter 1 Electricity and Metering Concepts
 - Voltage, Current, Phase
 - Power and Energy
 - Useful Triangles
 - The Electricity Meter
 - Vectors
 - Full Load Current
 - Meter Sockets
 - Instrument Transformers



Overview of the Pocket Guide

- Chapter 2 Meter Connection Diagrams
 - Service Types
 - Meter Form Selection
 - Meter Connection Diagrams



Overview of the Pocket Guide

- Chapter 3 Installing Meters
 - Meter Checks



Page 1 – Units, Power, & Energy

UNITS OF ELECTRICITY MEASUREMENT

	Unit	×1,000	×1,000,000
Current	ampere (A)	kA	
Potential difference	volt (V or E)	kV	-
Real power	watt (W)	kW	MW
Energy	watthour (Wh)	kWh	MWh
Reactive power	VAR (volt-ampere reactive)	kVAR	MVAR
Apparent power	volt-ampere (VA)	kVA.	MVA

POWER VS. ENERGY

Power Instantaneous rate at which work is done. 1 watt = the power expended when 1 ampere flows through 1 ohm. Measured by: watt meter. (Comparable to a speedometer.) Energy Average rate at which work is done multiplied by how long the power has been consumed. 1 watthour = the energy expended in one hour when the power is 1 watt. Measured by: watthour meter. (Comparable to an odometer.)



AC vs DC

Direct Current (DC) – an electric current that flows in one direction.(IEEE100)

 Alternating Current (AC) – an electric current that reverses direction at regularly recurring intervals of time. (IEEE100)



Ohm's Law



Georg Simon Ohm 1789 - 1854

Ohm's Law: Voltage = Resistance x Current V (or E) = I x R OR I = V / R



Power Law

Power Law for DC

Power (Watts) = Voltage x Current $P = V \times I$

Power Law for AC

Power = Voltage x Current x Power Factor P = V x I x PF

More on PF in a few minutes!







AC Theory Review – Sine Wave

Sine Wave





Basic AC Theory - Phase



Current is lagging Voltage by 30°



Basic AC Theory Power – The Simple View

V = Voltage (RMS)

I = Current (RMS)

PF = Power Factor

Power = Watts = V x I x PF

Power is sometimes referred to as Demand

Sinusoidal Waveforms Only

NO Harmonics

For a 120 Volt service drawing 13 Amps at Unity (1.0) PF, how much power is being drawn?

Power = 120 x 13 x 1.0 = 1560 Watts



Basic Meter Math Power – The Simple View

For a 120 Volt service drawing 13 Amps at 0.866 PF (Θ =30°), how much power is being drawn?

Power = $V \times I \times PF$

Power = 120 x 13 x 0.866 = 1351 Watts

For a 120 Volt service drawing 13 Amps at 0.5 PF (Θ =60°), how much power is being drawn?

Power = 120 x 13 x 0.5 = 780 Watts







Basic AC Theory Power – The Simple View

In the previous example we had:

Power = 120 x 13 x 0.866 = 1351 Watts

Normally we don't talk about Watts, we speak in Kilowatts

1000 Watts = 1 Kilowatt = 1 kW

Watts / 1000 = Kilowatts

For a 120 Volt service drawing 13 Amps at 0.866 PF, how <u>many Kilowatts</u> are being drawn?







Basic AC Theory Energy – What We Sell

If power is how fast water flows from a pipe, then energy is how much water we have in a bucket after the water has been flowing for a specified time.

Energy = Power x Time

1 kW for 1 Hour = 1 Kilowatt-Hour = 1 kWh

Energy (Wh) = $V \times I \times PF \times T$

where T = time in hours

Energy (kWh) = (V x I x PF / 1000) x T



Basic Meter Math Energy – What We Sell

For a 120 Volt service drawing 45 Amps at a Power Factor of 0.9 for 1 day, how much Energy (kWh) has been used?

Energy (kWh) = (V x I x PF / 1000) x T Energy = $(120 \times 45 \times 0.9 / 1000) \times 24 = 116.64$ kWh For a 240 Volt service drawing 60 Amps at a Power Factor of 1.0 for 5.5 hours, how much Energy (kWh) has been used?

Energy = (240 x 60 x 1.0 / 1000) x 5.5 = 79.2 kWh



Basic AC Theory What is VA?

Power was measured in Watts. Power does useful work. The power that does useful work is referred to as "Active Power".

VA is measured in Volt-Amperes. It is the capacity required to deliver the Power. It is also referred to as the "Apparent Power".

Power Factor = Active Power / Apparent Power

 $VA = V \times I$

PF = W / VA



Basic Meter Math Power – VA

For a 120 Volt service drawing 13 Amps at 0.5 PF (60°)

How much power is being drawn? Power = $120 \times 13 \times 0.5 = 780$ Watts How many VA are being drawn? VA = $120 \times 13 = 1560$ Volt-Amperes





Basic Meter Math Power – VA

For a 120 Volt service drawing 13 Amps at 0.866 PF (30°)

How much power is being drawn? Power = $120 \times 13 \times 0.866 = 1351$ Watts How many VA are being drawn? VA = $120 \times 13 = 1560$ Volt-Amperes





Basic Meter Math Power – VA

For a 120 Volt service drawing 13 Amps at 1.0 PF (0°)

How much power is being drawn? Power = $120 \times 13 \times 1.0 = 1560$ Watts How many VA are being drawn? VA = $120 \times 13 = 1560$ Volt-Amperes





Power Factor, Watts, and VA

For our 120V, 13A system

Phase Angle	PF	Watts	VA
0	1.0	1560 W	1560 VA
30	0.866	1351 W	1560 VA
60	0.5	780 W	1560 VA

As PF get closer to 1, the Watt value gets closer to the VA value! This means more real power is being consumed!

A table of PF vs phase angle values is on pages 18-19



Watt, VAR, and VA

Watt - useful power that does real work at the load – light a bulb or turn a motor

VAR – non-useful power that is required to drive the inductance or capacitance of a power line

VA – the total power in the system; the vector sum of Watts and VARs



Watt, VAR, and VA





Where do VARs come from?



Inductance in the power transmission line lower power factor and increases VARs!



Power Factor Definition:

Power Factor represents the ratio of active power (Watts) to the total power (VA) in a system.

It is a representation of the percentage of useful work being done.



Power Factor, Watts, and VARs

For a 120V, 13A System

Phase Angle	PF	Watts	VAR	VA
0	1	1560 W	0 VAR	1560 VA
30	0.866	1351 W	780 VAR	1560 VA
60	0.5	780 W	1351 VAR	1560 VA



Page 8 - Useful Triangles

THE RIGHT TRIANGLE



A right triangle is a triangle having one right angle (90°).

A relationship exists between the sides of every right triangle. Mathematically, this formula is:

 $c^2 = a^2 + b^2$

Fixed relationships also exist between two sides and one angle. These standard relationships, useful when solving AC circuit problems, are called trigonometric functions:

Sine A =
$$\frac{\text{opposite side}}{\text{hypotenuse}} = \frac{a}{c}$$

Cosine A = $\frac{\text{adjacent side}}{\text{hypotenuse}} = \frac{b}{c}$
Tangent A = $\frac{\text{opposite side}}{\text{adjacent side}} = \frac{a}{b}$



Page 9 - Useful Triangles

IMPEDANCE TRIANGLE

In AC circuits, three quantities limit the flow of current:

- Resistance R
- Inductive reactance X_L
- Capacitive reactance X_C





Resistive Load



Resistors are measured in Ohms. When an AC voltage is applied to a resistor, the current is in degrees. A resistive load is considered a "linear" load because when the voltage is sinusoidal the current is sinusoidal.



Inductive Load



Inductors are measured in Henries. When an AC voltage is applied to an inductor, the current is 90 degrees out of phase. We say the current "lags" the voltage. A inductive load is considered a "linear" load because when the voltage is sinusoidal the current is sinusoidal.



Capacitive Load



Capacitors are measured in Farads. When an AC voltage is applied to a capacitor, the current is 90 degrees out of phase. We say the current "leads" the voltage. A capacitive load is considered a "linear" load because when the voltage is sinusoidal the current is sinusoidal.



Page 10 - Power Triangle

(Sinusoidal Waveforms)

POWER TRIANGLE



Active power, also called working power or true power, is what wattmeters measure and is what most customers are billed for.

Apparent power is the total power generated by the utility.

Reactive power circulates in the wires, alternating between magnetic fields in inductive motor windings and transformers, and electrostatic fields in capacitors.

Active power divided by apparent power is the power factor of the circuit. It is also the cosine of the angle θ in the power triangle.





If V = Sin(ω t) and I = Sin(ω t - θ) (the load is linear) then

Active Power = $VICos(\theta)$ WattsReactive Power = $VISin(\theta)$ Volt-Amp Reactive (VAR)Apparent Power =VIVolt-Amp (VA)



Power Factor Definition





Page 14 – Vector (Phasor) Diagrams

VECTORS

Sine waves can represent AC voltages and currents, but except for the most simple circuits, they make circuit analysis messy and confusing. Vectors are usually used instead of sine waves. The length of the vector (arrow) illustrates the value of the electrical quantity – for example, how many volts. The angle of each vector shows its relationship, relative to other vectors in the circuit.



Vectors and Phasors are the same thing!



Vector Diagrams





 $V = 10Sin(2\pi ft - 30)$


Vector Diagrams

- The length of the vector is proportional to the value of the quantity
- The angle of the vector (by convention phase A is drawn as horizontal) shows the phase of the quantity relative to phase A voltage.
- Here the current "lags" the voltage by 30 degrees.



$$= 2.5\sqrt{2}Sin(2\pi ft - 30)$$



Vector Diagrams

• Vectors are particularly useful in poly-phase situations





Pages 20 – 21 Full Load Current

Single Phase Full Load Current = $\frac{circuit \ kVA \ x \ 10000}{circuit \ voltage}$

3 Phase Full Load Current = $\frac{kVA \ x \ 10000}{1.732 \ x \ voltage \ (L-L)}$

Full load Current Tables are given for standard size distribution transformers on pages 20 - 21



Page 85 – Allowable Ampacity

Co	nductor Si	ize		Aluminum or	
(AWG)	(kcmil)	Diameter (in.)	Copper (A)	Copper-Clad Aluminum (A)	
6		0.162	75	55	
4		0.204	95	75	
3		0.229	115	85	
2		0.258	130	100	
1		0.289	145	115	
0 (1/0)		0.325	170	135	
00 (2/0)		0.365	195	150	
000 (3/0)		0.410	225	175	
0000 (4/0)		0.460	260	205	
	250	0.500	290	230	
	300	0.548	320	260	
	350	0.592	350	280	
	400	0.632	380	305	
	500	0.707	430	350	

Maximum current-carrying capacity of conductors at 194°F (90°C) with THNN insulation. See also NEC Table 310.15(B)(16).



Page 22 – Meter Bases





Page 23 – Meter Sockets

Socket	Voltage	Current	Comment
For sing	le-phase circuits:		
(\cdot)	120/240V, 3-wire	Up to 200 amps	Direct-connect socket
(· · ·)	120/208V, 3-wire	Up to 200 amps	Direct-connect socket
(¹ , ¹)	120/240V, 3-wire	201-320 amps	Direct-connect 320A socket
(; ; ; ; ; ; ; ; ; ; ; ; ; ; ; ; ; ; ;	120/240V, 3-wire	Above 200 amps	With CTs



Page 23 – Meter Sockets

For three-phase circuits:



120/208V, 4-wire 120/240V, 4-wire 277/480V, 4-wire Up to 200 amps

Direct-connect socket



120/208V, 4-wire 120/240V, 4-wire 277/480V, 4-wire Above 200 amps With CTs



Page 25 – Meter Class

METER CLASS

The meter Class (CL) designates the upper limit of the load current, in amperes.

Class			Test Current (TA)		
	Maximum Current	Meter Type	Full Load	Light Load	50% PF
10	10A	Instrument-rated	2.5A	0.25A	2.5A
20	20A	Instrument-rated	2.5A	0.25A	2.5A
100	100A	Self-contained	15.0A	1.50A	15.0A
200	200A	Self-contained	30.0A	3.00A	30.0A
320	320A	Self-contained	50.0A	5.00A	50.0A

Test current for meter classes is defined in ANSI C12.1.



Page 25 – Meter Voltages

METER VOLTAGE, FREQUENCY

Standard voltage ratings assigned to meters are:

72 volts 120 volts 240 volts 277 volts 480 volts 600 volts

The use of 600-volt meters is limited for safety considerations. Meters for 72 volts are used only for special applications.

Some electronic meters can operate over a broad range of voltages, for example: from 120V to 277V or from 120V to 480V.

Meters manufactured for installation in North America are rated for use at 60 hertz.



What is a Transformer?

 A TRANSFORMER is a device used to change the voltage levels of electricity to facilitate the transfer of electricity from generating stations to customers. A step-up transformer increases the voltage while a step-down transformer decreases it. www.duquesnelight.com/understandingelectr icityupdate/electricterms.html





Basic Transformer Theory

- Vp = primary voltage
- Ip = primary current
- Np = primary turns
- Pp = primary power
- Vs = secondary voltage
- Is = secondary current
- Ns = secondary turns
- Ps = secondary power
 This is true for an IDEAL transformer!



$$Is = \frac{Np}{Ns} Ip$$

$$Pp = Vp \bullet Ip = Ps = Vs \bullet Is$$



What is an Instrument Transformer?

Instrument Transformers convert signal levels from dangerous (high voltage) or inconvenient (high current, or current at high voltage) to levels appropriate for metering.

- There are two fundamental types:
- CTs (Current Transformers)
- PTs (Potential Transformers)





Page 26 & 27 CTs and PTs (VTs)





Other symbols used for CTs



Other symbols used for VTs



Page 28 Transformer Rated Site



Watthours = register reading \times CTR \times VTR \times Dial K Example: A CT with a ratio of 400:5 and a VT with a ratio of 20:1 are installed with a watthour meter with a Dial K of 1. The meter reading is 96 kilowatt-hours.

Energy =
$$96 \times \frac{400}{5} \times \frac{20}{1} \times 1 = 153,600 \text{ kWh}$$



Page 29 Safety Tips

- Measure for hazardous voltage before installing a jumper between any two points.
- When conditions present hazards, do not work alone. When servicing or adjusting meters, have a partner nearby in case assistance is needed.
- If a meter falls, do not attempt to catch it. Trying to catch a glasscovered meter can result in cuts to hands or arms.
- When working with current transformers and voltage transformers:
 - Do not open the secondary circuit of a CT if current may be flowing in the primary. The voltage across the secondary will increase rapidly toward infinity, risking serious personal injury, and the CT might explode.
 - Do not short the secondary circuit of a VT. The resulting electric flash can cause serious injury.
 - Wire to ground, the proper secondary terminals of CTs and VTs.



Page 29 Safety Tips

- Wear gloves and eye protection, goggles, or a face shield when setting or removing a meter. Keep co-workers clear.
- Do not use an air hose to clean clothing, hair, hands, or areas of the shop.
- Keep work areas neat and tidy.
- · Use tongs, not fingers, to dip parts in cleaning fluids.
- · When conducting high-potential (high-pot) tests on insulation:
 - One person per test set; all others stand clear.
 - Wear 10 kV rubber gloves.
 - Use one hand only to avoid a possible electrical path through your heart.
- Above all, follow all your company's established operating and safety procedures.



Meter Form Selection





Meter Form Selection





Page 30 Meter Form Designation

FORM DESIGNATION

Meter forms are defined in ANSI standard C12.10. As an example, Form 5S is illustrated below. Meters from different manufacturers with the same form and rating voltage are interchangeable. The meter form:

Specifies the internal meter wiring, terminals.





Page 31 Meter Form Designation

Form Designation	No. of Stators	No. of Current Circuits Inside Meter	No. of External Current Wires Connected To Meter	
Socket Meters				
1S	1	1	2	
2S	1	2	3	
3S	1	1	2	
4S	1	2	3	
5S	2	2	3	(or 4)
6S	2	3	4	wye
8S	2.	3	4	delta
9 S	3	3	4	wye
12S	2	2	3	
14S	2	3	4	wye
15S	2	3	4	delta
16S	3	3	4	wye
36S	2	2	3	
45S	2	2	4	wye



Common Meter Forms

Self Contained

Meter Form	# Wires	# Elements	# Phases	Delta / Wye	Class
1S	2	1	1	N/A	200
2S	3	1	1	N/A	200/320
12S	3	2	2	Delta	200/320
16S	4	3	3	Wye	200/320
16S	4	3	3	Delta	200/320



Common Meter Forms

Transformer Rated

Meter Form	# Wires	# Elements	# Phases	Delta / Wye	Class
3S	2	1	1	N/A	20
5S	3 or 4	2	3	Delta	20
6S	4	2.5	2	Wye	20
9S	4	3	3	Wye	20



Page 32 Distribution Circuit Symbols



Three-wire network ↓ 1

120 volts line-to-neutral 208 volts line-to-line



Page 32 Distribution Circuit Symbols

Three-wire Three-phase delta

240 volts line-to-line or 480 volts line-to-line

Four-wire Three-phase delta



240 volts line-to-line 120 volts adjacent-line to neutral 208 volts opposite-line to neutral

Four-wire Three-phase wye







Pages 33-34 Meter Diagram Symbols





Current transformer, 2-wire with polarity marks Current transformer, 3-wire with polarity marks Voltage transformer with polarity marks

Meter

Current coil

Voltage coil



Page 35 Meter Diagram Index

	Circuit	Voltage	Current Connections	Meter Form	Page
1254	2-wire, 1-phase	120	Self-contained	15	34
k-Pl	3-wire, 1-phase	120/240	Self-contained	2S	35
Sing			With CTs	3S, 4S, 4A	36-38
work	3-wire network	100,000	Self-contained	12\$	39
Neth		120/208	With CTs	5S, 5A	40-41
	3-wire delta	240/480/120	Self-contained	12\$	46
			With CTs	5S, 5A	42-43
		With VTs	With CTs	5S, 5A	44-45
	4-wire delta	240/120/208	Self-contained	15S, 15A	47-48
			With CTs	5S, 5A, 8S, 8A	49-52
				9S, 45S	53-54
phase	4-wire wye	208/120, 480/277	Self-contained	14S, 14A,	07 70
Poly F				16S, 16A	0/-/0
1.44			With CTs	5S, 5A, 6S,	55-58
				6A, 9S	61,64
		With VTs	With CTs	5S, 5A	59-60
				6S, 6A	62-63
				9S, 9A	65-66
				36S, 45S	71-72



Page 37 Form 2S – SC Single Phase 3W





Page 37 Form 2S – SC Single Phase 3W





Page 39 Form 4S – TR Single Phase 3W



120 volts line-to-neutral 240 volts line-to-line





Page 39 Form 4S – TR Single Phase 3W





Page 41 Form 12S – SC 3W Network

Three-Wire Network



120 volts line-to-neutral 208 volts line-to-line





Page 41 Form 12S – SC 3W Network





Page 42 Form 5S – TR 3W Network

Three-Wire Network With Two CTs

2 I

120 volts line-to-neutral 208 volts line-to-line





Page 42 Form 5S – TR 3W Network





Page 48 Form 12S – SC 3WD

Three-Phase Three-Wire Delta



240 volts line-to-line or 480 volts line-to-line or 120 volts line-to-line





Page 48 Form 12S – SC 3WD




Page 44 Form 5S – TR 3WD

Three-Phase Three-Wire Delta With Two CTs



240 volts line-to-line or 480 volts line-to-line or 120 volts line-to-line









Page 71 Form 16S – SC 4WY

Three-Phase Four-Wire Wye



208 volts line-to-line 120 volts line-to-neutral or 480 volts line-to-line 277 volts line-to-neutral





Page 71 Form 16S – SC 4WY





Page 67 Form 9S – TR 4WY





For high voltages. The VTs apply reduced voltages to the meter.





Page 67 Form 9S – TR 4WY





Page 87 Meter Socket Checks

The checks on pages 87 through 94 will determine if the socket is wired correctly, or if conditions must be corrected before setting the meter.

Use a fused jumper when making socket meter checks. If accidental contact is made with a voltage, the fuse will blow. To make a fused jumper, install a 1-amp fuse in series with the jumper wires.



Be alert for backfeed. If line voltage is on a load-side terminal, backfeed exists. Check for temporary power still connected, in-feed from solar panels or other generators, and energy diversion. Note: "Green" power makes backfeed more likely.

Use extra caution when 480 volts or higher might be present.



Page 87 Meter Socket Checks

Visual Checks

Before making electrical checks, make these visual checks:

- Socket is firmly mounted and vertical.
- Jaws and terminals are secure.
- Socket jaws are not sprung.
- Conductors are not under undue strain at their terminals.
- Strands have not been removed to squeeze conductors into under-sized terminals.
- Electrical connections are tight.
- There is no possibility of shorting or grounding when the meter is installed.
- · Voltmeter leads and clips are in first-class condition.



Page 89 Single Phase 3W Meter Check

Single-Phase, Three-Wire

For 240/480V services, double the voltage readings in these checks.



Check 1. Line-side voltage A to B = 240 volts

A to Neutral = 120 volts B to Neutral = 120 volts

Check 2. Backfeed

a to Neutral = 0 volts b to Neutral = 0 volts

Voltage reading other than 0 indicates backfeed from the load side. Do not continue until condition is corrected.



Page 89 Single Phase 3W Meter Check

Check 3. Load-side fault

A to a = 0 volts B to b = 0 volts

Voltage reading other than 0 indicates a fault from a to N, or b to N. Do not set meter until condition is corrected.

Add temporary jumper - Neutral to b A to b = 120 volts

Checks the jumper connections before proceeding.

A to a = 0 volts

Voltage reading other than 0 indicates a fault from a to b. Do not set meter until condition is corrected.

Remove jumper.

Use a fused jumper when making socket meter checks.





Questions? Comments? Want a copy of this presentation? Go to powermetrix.com/presentations/

Thank you for your time!



